

PROJECT WORK

"Verilog Implementation of Digital Circuit Designs on FPGA using Vivado"


Topic: Traffic Light Controller Design using Verilog



 PROBLEM STATEMENT


The aim of the project is to design a traffic controller for a T-intersection.

Let's understand the problem statement through the image given below.



The six cases present here eventually turn to the six states .

This is the state diagram:

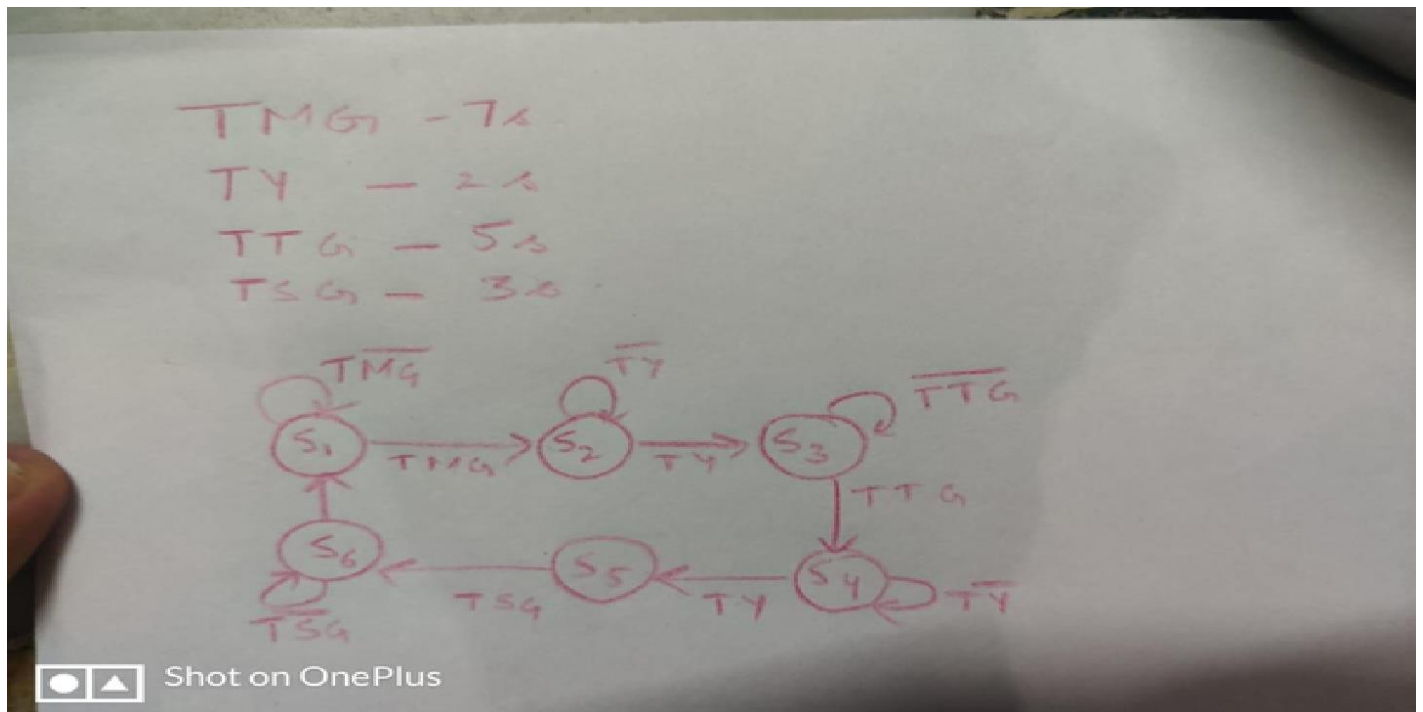

From the state diagram we for the state table:

State Table

Present state ABC	Input	NS A ⁺ B ⁺ C ⁺		M1 RYG	M2 RYG	T RYG	S RYG	
001	$\overline{T}Y$	001	}	001	001	100	100	
001	TY	010						
010	$\overline{T}Y$	010	}	001	010	100	100	
	TY	011						
011	$\overline{T}Y$	011	}	001	100	001	100	
	TY	100						
100	$\overline{T}Y$	100	}	010	100	010	100	
	TY	101						
101	$\overline{T}Y$	101	}	100	100	100	001	
	TY	110						
110	$\overline{T}Y$	110	}	100	100	100	010	
	TY	001						
111	-	000		000	000	000	000	

VERILOG CODE

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer:
```

```
//
```

```
// Create Date: 16.07.2020 12:53:25
```

```
// Design Name:
```

```
// Module Name: Traffic_Light_Controller
```

```
// Project Name:
```

```
// Target Devices:
```

```
// Tool Versions:
```

```
// Description:
```

```
//
```

```
// Dependencies:
```

```
//
```

```
// Revision:
```

```
// Revision 0.01 - File Created
```

```
// Additional Comments:
```

```
//
```

```
////////////////////////////////////////////////////////////////
```

```
module Traffic_Light_Controller(
```

```
    input clk,rst,
```

```
    output reg [2:0]light_M1,
```

```
    output reg [2:0]light_S,
```

```
    output reg [2:0]light_MT,
```

```
output reg [2:0]light_M2
```

```
);
```

```
parameter S1=0, S2=1, S3 =2, S4=3, S5=4,S6=5;
```

```
reg [3:0]count;
```

```
reg[2:0] ps;
```

```
parameter sec7=7,sec5=5,sec2=2,sec3=3;
```

```
always@(posedge clk or posedge rst)
```

```
begin
```

```
if(rst==1)
```

```
begin
```

```
ps<=S1;
```

```
count<=0;
```

```
end
```

```
else
```

```
case(ps)
```

```
  S1: if(count<sec7)
```

```
    begin
```

```
      ps<=S1;
```

```
      count<=count+1;
```

```
    end
```

```
  else
```

```
    begin
```

```
ps<=S2;  
count<=0;  
end
```

```
S2: if(count<sec2)  
    begin  
        ps<=S2;  
        count<=count+1;  
    end
```

```
else  
    begin  
        ps<=S3;  
        count<=0;  
    end
```

```
S3: if(count<sec5)  
    begin  
        ps<=S3;  
        count<=count+1;  
    end
```

```
else  
    begin  
        ps<=S4;  
        count<=0;  
    end
```

```
S4: if(count<sec2)  
    begin  
        ps<=S4;  
        count<=count+1;  
    end
```

```
else
    begin
        ps<=S5;
        count<=0;
    end
S5:if(count<sec3)
    begin
        ps<=S5;
        count<=count+1;
    end

else
    begin
        ps<=S6;
        count<=0;
    end

S6:if(count<sec2)
    begin
        ps<=S6;
        count<=count+1;
    end

else
    begin
        ps<=S1;
        count<=0;
    end
default: ps<=S1;
```

```

        endcase
    end

    always@(ps)
    begin
        case(ps)

            S1:
            begin
                light_M1<=3'b001;
                light_M2<=3'b001;
                light_MT<=3'b100;
                light_S<=3'b100;
            end
            S2:
            begin
                light_M1<=3'b001;
                light_M2<=3'b010;
                light_MT<=3'b100;
                light_S<=3'b100;
            end
            S3:
            begin
                light_M1<=3'b001;
                light_M2<=3'b100;
                light_MT<=3'b001;
                light_S<=3'b100;
            end
            S4:
            begin

```




```

        light_M1<=3'b010;
        light_M2<=3'b100;
        light_MT<=3'b010;
        light_S<=3'b100;
    end
S5:
begin
    light_M1<=3'b100;
    light_M2<=3'b100;
    light_MT<=3'b100;
    light_S<=3'b001;
end
S6:
begin
    light_M1<=3'b100;
    light_M2<=3'b100;
    light_MT<=3'b100;
    light_S<=3'b100;
end
default:
begin
    light_M1<=3'b000;
    light_M2<=3'b000;
    light_MT<=3'b000;
    light_S<=3'b010;
end
endcase
end

endmodule

```

RTL-SCHEMATIC

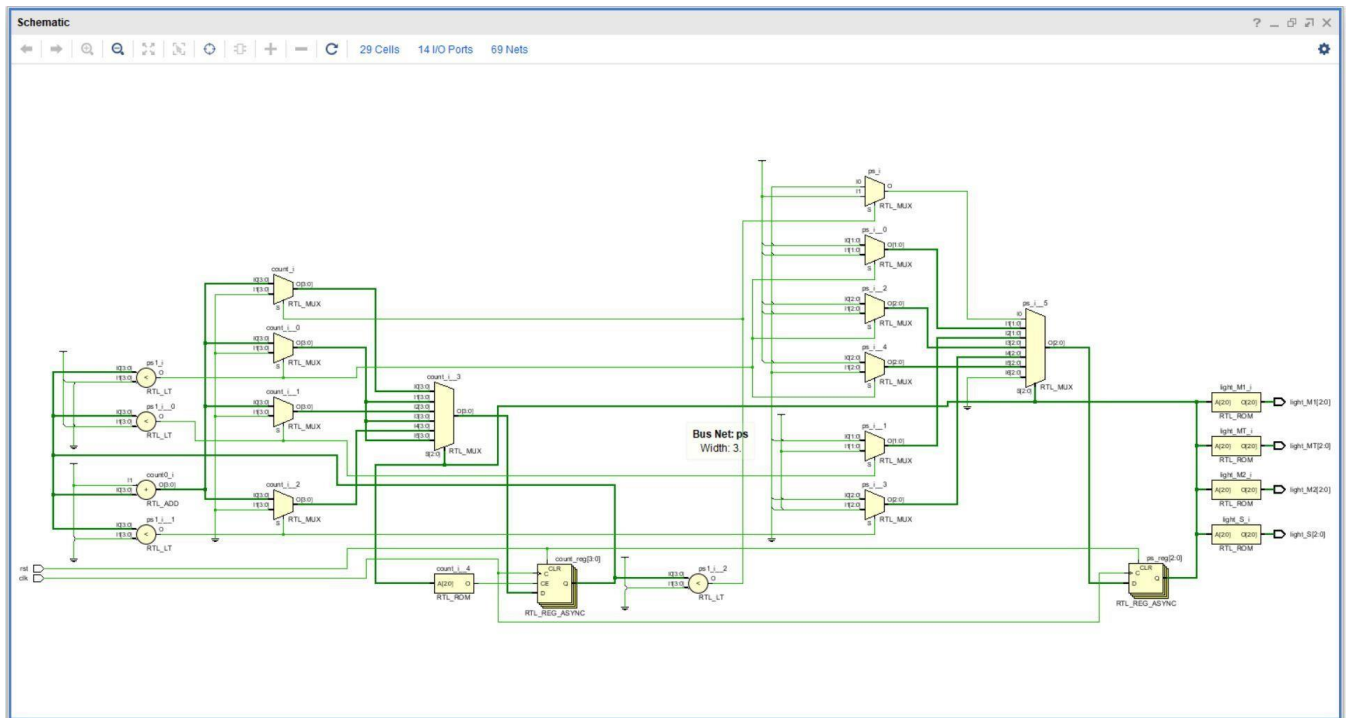

TESTBENCH

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer:
```

```
//
```

```
// Create Date: 16.07.2020 23:44:40
```

```
// Design Name:
```

```
// Module Name: Traffic_Light_Controller_TB
```

```
// Project Name:
```

```
// Target Devices:
```

```
// Tool Versions:
```

```
// Description:
```

```
//
```

```
// Dependencies:
```

```
//
```

```
// Revision:
```

```
// Revision 0.01 - File Created
```

```
// Additional Comments:
```

```
//
```

```
////////////////////////////////////////////////////////////////
```

```
module Traffic_Light_Controller_TB;
```

```
reg clk,rst;
```

```
wire [2:0]light_M1;
```

```
wire [2:0]light_S;
```

```
wire [2:0]light_MT;
```

```
wire [2:0]light_M2;
```

```
Traffic_Light_Controller dut(.clk(clk) , .rst(rst) , .light_M1(light_M1) , .light_S(light_S)  
.,light_M2(light_M2),.light_MT(light_MT) );
```

```
initial
```

```
begin
```

```
    clk=1'b0;
```

```
    forever #(1000000000/2) clk=~clk;
```

```
end
```

```
initial
```

```
begin
```

```
    rst=0;
```

```
    #1000000000;
```

```
    rst=1;
```

```
    #1000000000;
```

```
    rst=0;
```

```
    #(1000000000*200);
```

```
    $finish;
```

```
end
```

```
endmodule
```

SIMULATED WAVEFORM




Upon analysing the waveform we can clearly see that the FSM works perfectly.

IO PORT ASSIGNMENT

I/O Ports												
Name	Direction	Neg Diff Pair	Package Pin	Fixed	Bank	I/O Std	Vcco	Vref	Drive Strength	Slew Type	Pull Type	
All ports (14)												
light_M1 (3)	OUT			✓	15	LVCN0533*	3.300		12	SLOW	NONE	
light_M1[2]	OUT		H17	✓	15	LVCN0533*	3.300		12	SLOW	NONE	
light_M1[1]	OUT		K15	✓	15	LVCN0533*	3.300		12	SLOW	NONE	
light_M1[0]	OUT		J13	✓	15	LVCN0533*	3.300		12	SLOW	NONE	
light_M2 (3)	OUT			✓	14	LVCN0533*	3.300		12	SLOW	NONE	
light_M2[2]	OUT		N14	✓	14	LVCN0533*	3.300		12	SLOW	NONE	
light_M2[1]	OUT		R18	✓	14	LVCN0533*	3.300		12	SLOW	NONE	
light_M2[0]	OUT		V17	✓	14	LVCN0533*	3.300		12	SLOW	NONE	
light_MT (3)	OUT			✓	14	LVCN0533*	3.300		12	SLOW	NONE	
light_MT[2]	OUT		U17	✓	14	LVCN0533*	3.300		12	SLOW	NONE	
light_MT[1]	OUT		V16	✓	14	LVCN0533*	3.300		12	SLOW	NONE	
light_MT[0]	OUT		T15	✓	14	LVCN0533*	3.300		12	SLOW	NONE	
light_S (3)	OUT			✓	14	LVCN0533*	3.300		12	SLOW	NONE	
light_S[2]	OUT		U14	✓	14	LVCN0533*	3.300		12	SLOW	NONE	
light_S[1]	OUT		T16	✓	14	LVCN0533*	3.300		12	SLOW	NONE	
light_S[0]	OUT		V15	✓	14	LVCN0533*	3.300		12	SLOW	NONE	
Scalar ports (2)												

The ports are assigned from the ucf file .

SCHEMATIC AFTER SYNTHESIS

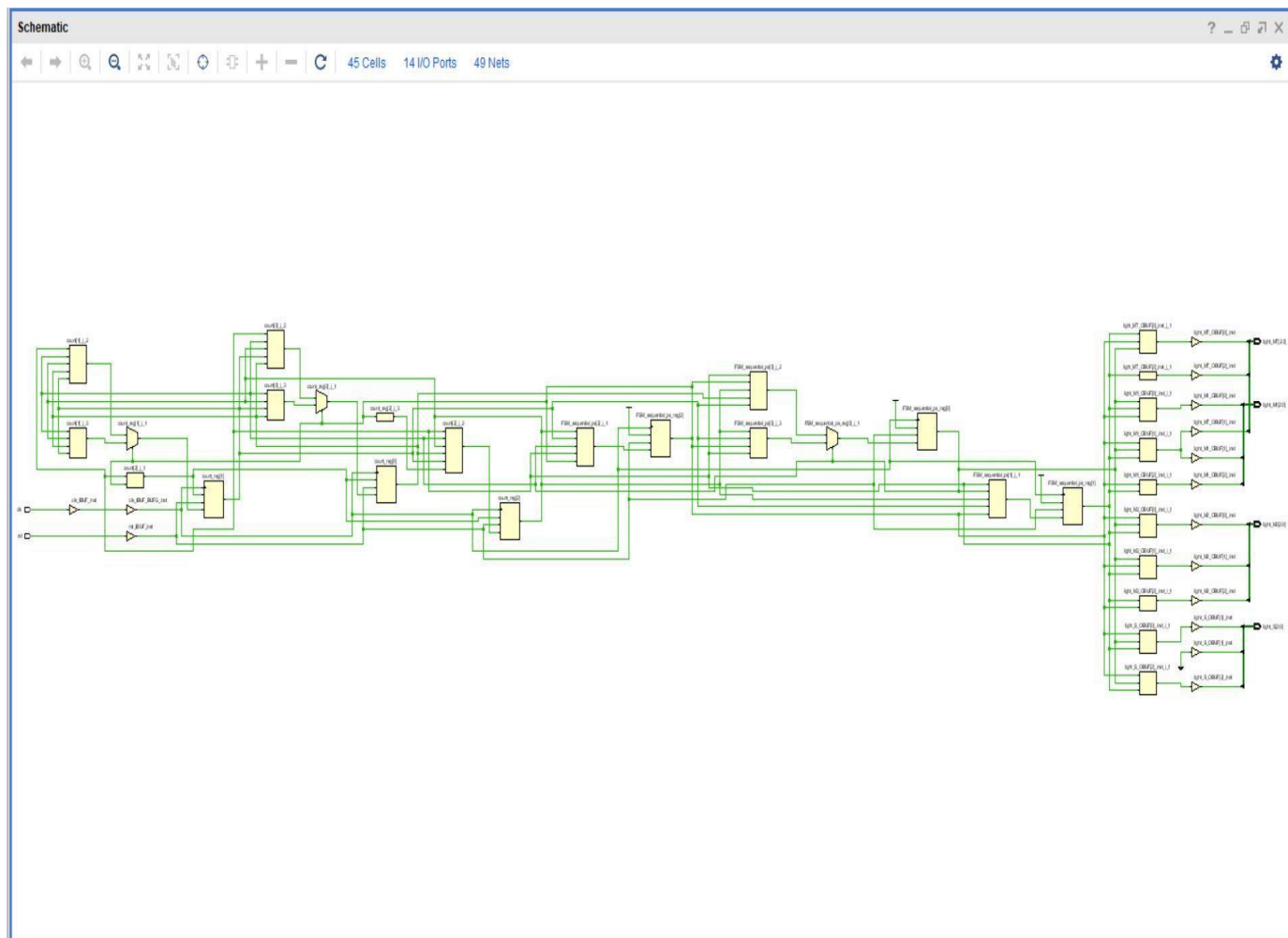

REPORTS AFTER SYNTHESIS

TIMING REPORT

Tcl Console

Messages

Log

Reports

Design Runs

Timing

?

—

□

✕

Q

≡

⏮

⏪

⏩

⏭

📁

»

Design Timing Summary

»

General Information

Timer Settings

Design Timing Summary

Check Timing (33)

Intra-Clock Paths

Inter-Clock Paths

Other Path Groups

User Ignored Paths

Unconstrained Paths

Setup

Hold

Pulse Width

Worst Negative Slack (WNS):

inf

Worst Hold Slack (WHS):

inf

Worst Pulse Width Slack (WPWS):

NA

Total Negative Slack (TNS):

0.000 ns

Total Hold Slack (THS):

0.000 ns

Total Pulse Width Negative Slack (TPWS):

NA

Number of Failing Endpoints:

0

Number of Failing Endpoints:

0

Number of Failing Endpoints:

NA

Total Number of Endpoints:

26

Total Number of Endpoints:

26

Total Number of Endpoints:

NA


There are no user specified timing constraints.

Timing Summary - timing_1


NOISE REPORT

Tcl Console	Messages	Log	Reports	Design Runs	Methodology	DRC	Noise	Timing	
Summary									
Messages (1)									
I/O Bank Details									
Links									
Name	Port	I/O Std	Vcco	Slew	Drive Strength (...)	Off-Chip Termina...	Remaining Margin ...	Notes	
I/O Bank 0 (0)									
I/O Bank 14 (9)									
V17	light_M2[0]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	83.71		
R18	light_M2[1]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	93.97		
N14	light_M2[2]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	96.99		
T15	light_MT[0]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	84.59		
V16	light_MT[1]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	73.29		
U17	light_MT[2]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	72.46		
V15	light_S[0]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	73.62		
T16	light_S[1]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	73.06		
U14	light_S[2]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	90.26		
I/O Bank 15 (3)									
J13	light_M1[0]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	88.79		
K15	light_M1[1]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	91.60		
H17	light_M1[2]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	91.35		
I/O Bank 16 (0)									
I/O Bank 34 (0)									
I/O Bank 35 (0)									


UTILIZATION REPORT

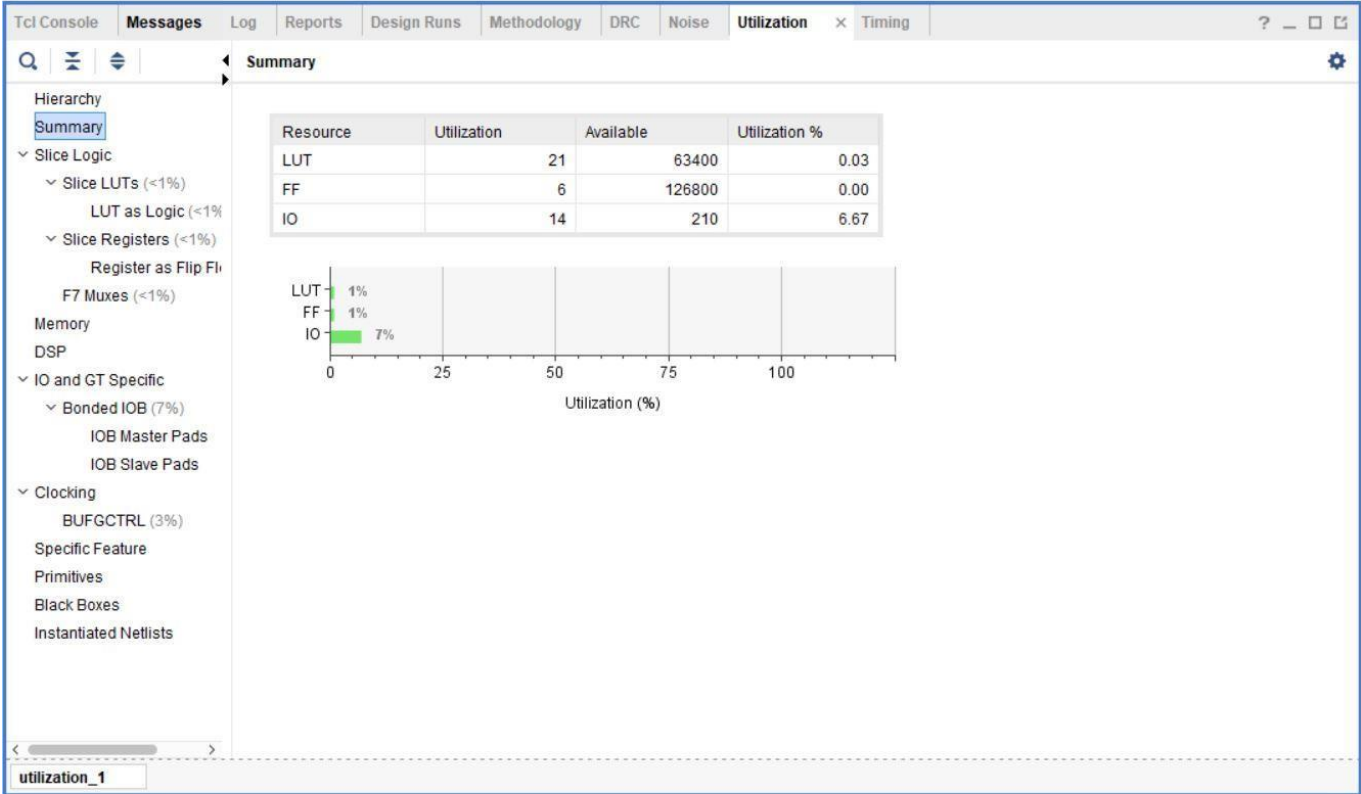


POWER REPORT

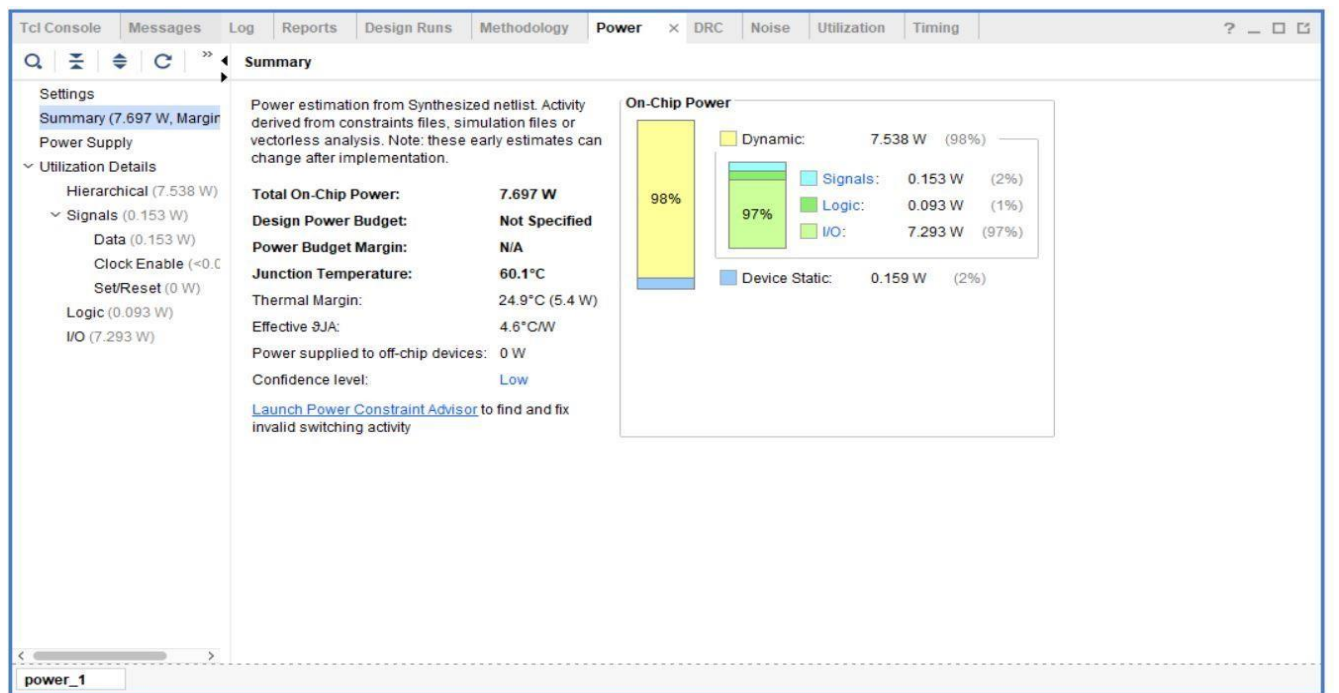


SCHEMATIC AFTER IMPLEMENTATION

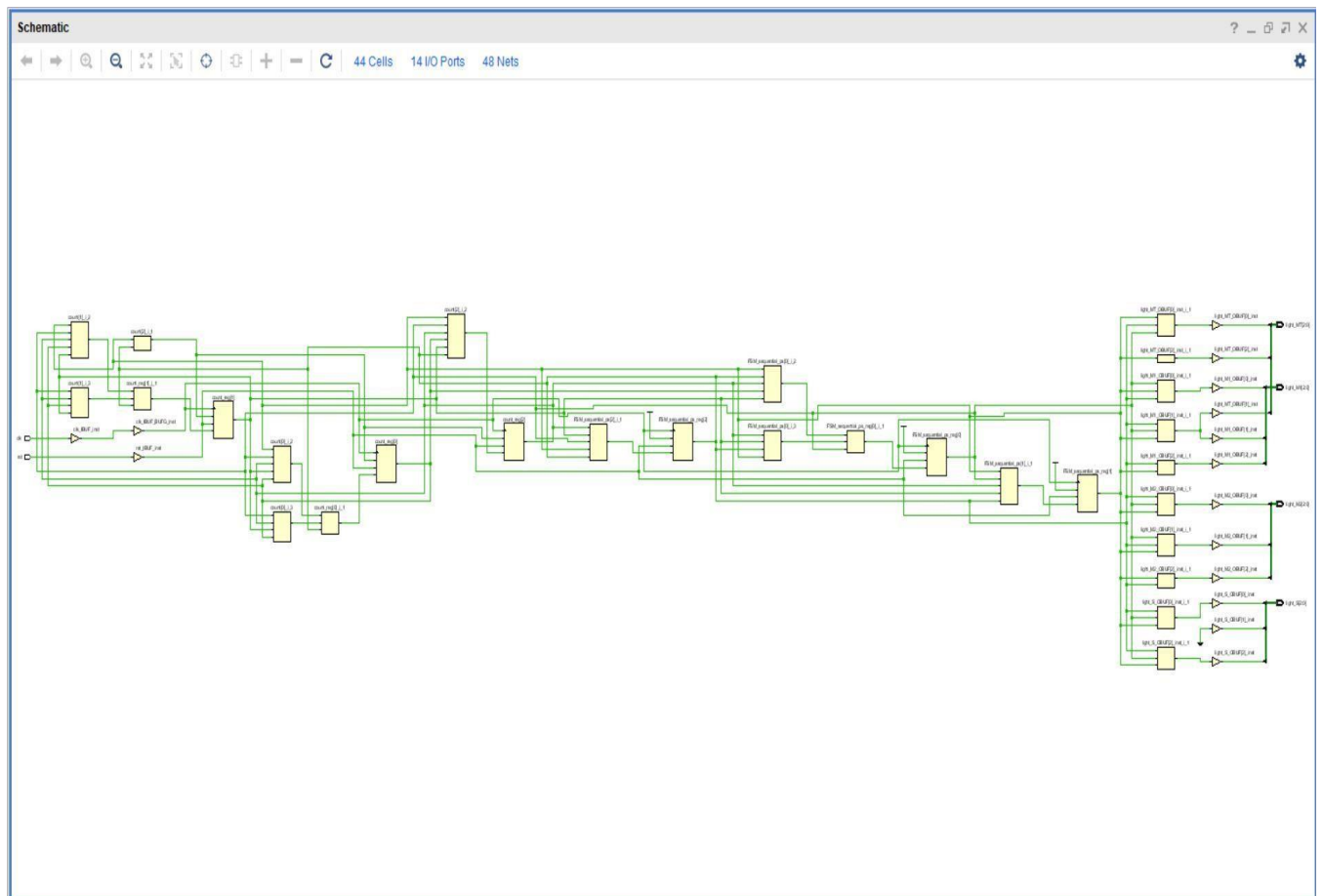

DEVICE LAYOUT AFTER IMPLEMENTATION

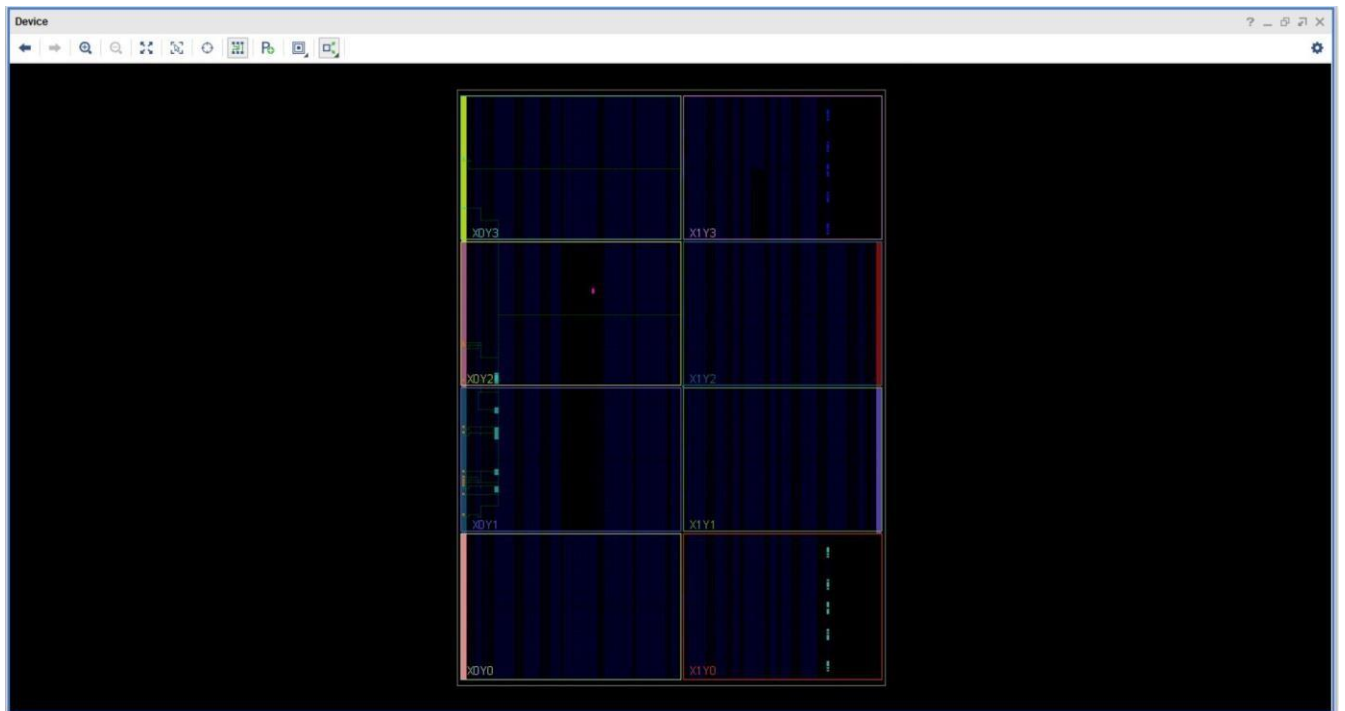

ZOOM IN VIEW

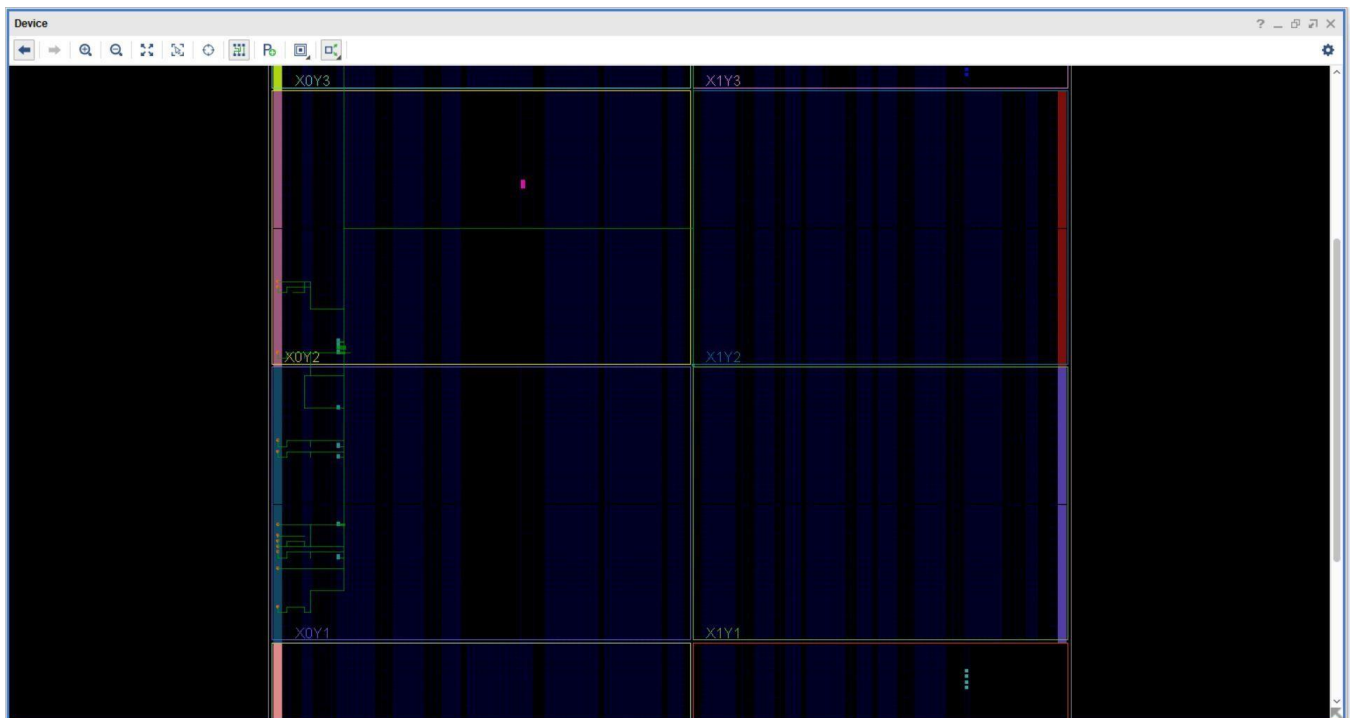

TIMING REPORT

Tcl Console

Messages

Log

Reports

Design Runs

Power

DRC

Methodology

Timing x

?

—

□

✖

Q

≡

⏮

↺

⏭

⏪

⏩

⏴

⏵

»

«

Design Timing Summary

General Information

Timer Settings

Design Timing Summary

Check Timing (33)

Intra-Clock Paths

Inter-Clock Paths

Other Path Groups

User Ignored Paths

Unconstrained Paths

Setup

Hold

Pulse Width

Worst Negative Slack (WNS): inf

Worst Hold Slack (WHS): inf

Worst Pulse Width Slack (WPWS): NA

Total Negative Slack (TNS): 0.000 ns

Total Hold Slack (THS): 0.000 ns

Total Pulse Width Negative Slack (TPWS): NA

Number of Failing Endpoints: 0

Number of Failing Endpoints: 0

Number of Failing Endpoints: NA

Total Number of Endpoints: 26

Total Number of Endpoints: 26

Total Number of Endpoints: NA

There are no user specified timing constraints.

Timing Summary - Impl 1 (saved) x

Timing Summary - timing 1 x

NOISE REPORT

Tcl Console

Messages

Log

Reports

Design Runs

Power

DRC

Methodology

Noise

Timing

?

_

□

✕

Summary

Messages (1)

I/O Bank Details

Links

Q

≡

⚙


I/O Bank Details

⚙


Name	Port	I/O Std	Vcco	Slew	Drive Strength (...)	Off-Chip Termina...	Remaining Margin ...	Notes
I/O Bank 0 (0)								
I/O Bank 14 (9)								
V17	light_M2[0]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	83.71	
R18	light_M2[1]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	93.97	
N14	light_M2[2]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	96.99	
T15	light_MT[0]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	84.59	
V16	light_MT[1]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	73.29	
U17	light_MT[2]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	72.46	
V15	light_S[0]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	73.62	
T16	light_S[1]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	73.06	
U14	light_S[2]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	90.26	
I/O Bank 15 (3)								
J13	light_M1[0]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	88.79	
K15	light_M1[1]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	91.60	
H17	light_M1[2]	LVC MOS33	3.30	SLOW	12	FP_VTT_50	91.35	
I/O Bank 16 (0)								
I/O Bank 34 (0)								
I/O Bank 35 (0)								

ssn_1

UTILIZATION REPORT

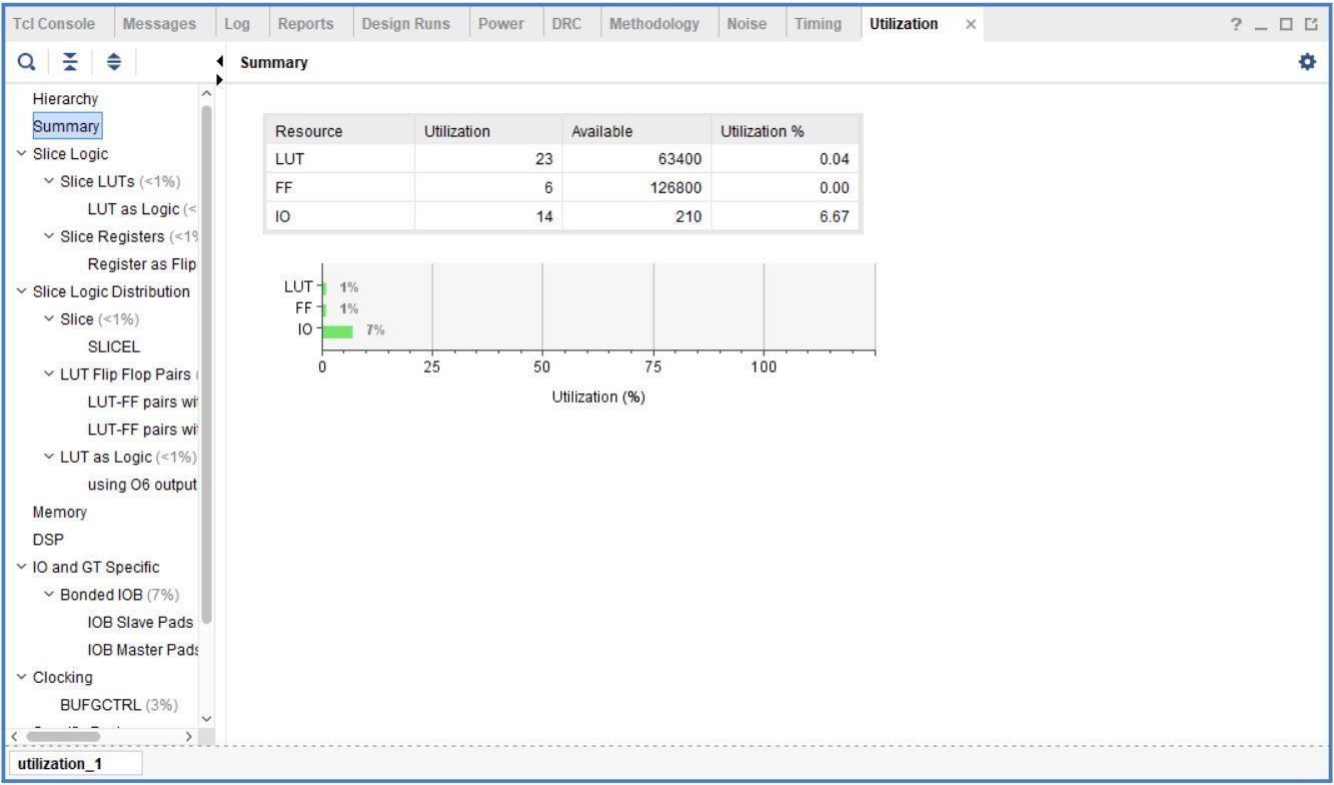

POWER REPORT

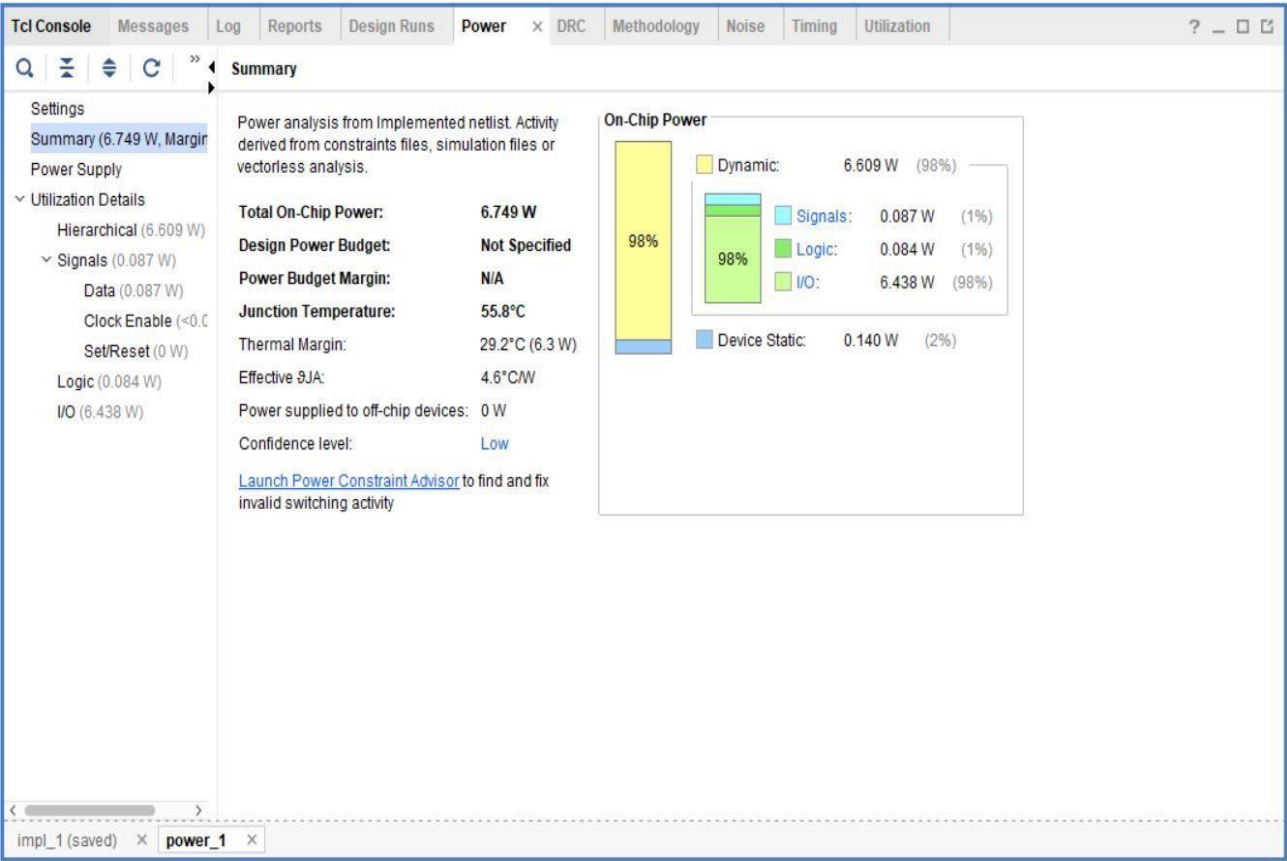

REFERENCES:

- 1) Ucf file for io assignment.
- 2) Nptel lectures on Digital design by prof. Srinivasan
- 3) Pdf given by Prof. Poonam Kasturi
- 4) http://www.asic-world.com/tidbits/verilog_fsm.html